

# Analog-12.7-10

Hiba Muhammed  
EE23BTECH11026

February 12, 2024

## Problem Statement

A radio can tune over the frequency range of a portion of the MW broadcast band: (800 kHz to 1200 kHz). If its LC circuit has an effective inductance ( $L$ ) and a variable capacitor with capacitance ( $C$ ), what must be the range of  $C$ ?